

Architecture, Programming, and Interfacing

Barry B. Brey

Chapter 10: Memory Interface

Introduction

- Simple or complex, every microprocessor-based system has a memory system.
- Almost all systems contain two main types of memory: **read-only memory** (ROM) and **random access memory** (RAM) or read/write memory.
- This chapter explains how to **interface** both memory types to the Intel family of microprocessors.

Chapter Objectives

Upon completion of this chapter, you will be able to:

- Decode the memory address and use the outputs of the decoder to select various memory components.
- Use **p**rogrammable **l**ogic **d**evices (**PLDs**) to decode memory addresses.
- Explain how to **interface** both RAM and ROM to a microprocessor.

Chapter Objectives

(*cont.*)


Upon completion of this chapter, you will be able to:

- Explain how **error correction code (ECC)** is used with memory.
- Interface memory to an **8-, 16-, 32-, and 64-bit** data bus.

10–1 MEMORY DEVICES

- Before attempting to interface memory to the microprocessor, it is essential to understand the operation of memory components.
- In this section, we explain functions of the four common types of memory:
 - Read-only memory (**ROM**)
 - Flash memory (**EEPROM**)
 - Static random access memory (**SRAM**)
 - Dynamic random access memory (**DRAM**)

Memory Pin Connections

 

- address inputs
- data outputs or input/outputs
- some type of selection input
- at least one control input to select a **read** or **write** operation

Figure 10–1 A pseudo memory component illustrating the address, data, and control connections.

Address Connections

- Memory devices have address inputs to select a memory location within the device.
- Almost always labeled from A_0 , the least significant address input, to A_n
 - where subscript n can be any value
 - always labeled as one less than total number of address pins
- A memory device with **10 address pins** has its address pins labeled from A_0 to A_9 .

Address Space (Main Memory: RAM)

- Address bus:10 bit → Address Space:1 Kbytes (2^{10})
- Address bus:11 bit → Address Space:2 Kbytes (2^{11})
- Address bus:16 bit → Address Space:64 KBytes (2^{16})
- Address bus:20 bit → Address Space:1 MBytes
- Address bus:32 bit → Address Space:4 GBytes
- Address bus:34 bit → Address Space:16GBytes
- Address bus:36 bit → Address Space:64GBytes
- Address bus:38 bit → Address Space:256GBytes
- Address bus:52 bit → Address Space: 10^{15} Bytes

- The number of address pins on a memory device is determined by the number of memory locations found within it.
- A 1K memory device has **10 address pins**.
 - therefore, 10 address inputs are required to select any of its **1024** memory locations

Data Connections

- All memory devices have a set of data outputs or input/outputs.
 - today, many devices have **bidirectional** common I/O pins
 - data connections are points at which data are entered for storage or extracted for reading
- Data pins on memory devices are labeled D_0 through D_7 for an 8-bit-wide memory device.

Selection Connections

- Each memory device has an input that selects or enables the memory device.
 - sometimes more than one
- This type of input is most often called a **chip select** (\overline{CS}) **chip enable** (\overline{CE}) or simply **select** (\overline{S}) input.

Control Connections

- All memory devices have some form of control input or inputs.
 - ROM usually has one control input, while RAM often has one or two control inputs
- Control input often found on ROM is the **output enable** or **gate** connection, which **allows data flow** from output data pins.
- The $\overline{\text{OE}}$ connection enables and disables a set of **three-state buffers** located in the device and must be active to read data.

- RAM has either one or two control inputs.
 - if one control input, it is often called $\overline{R/\bar{W}}$
- If the RAM has two control inputs, they are usually labeled \overline{WE} (or \bar{W}), and \overline{OE} (or \bar{G}).
 - **write enable** must be active to perform memory write, and \overline{OE} active to perform a memory read
 - when the two controls are present, they must never both be active at the same time
- If both inputs are inactive, data are neither written nor read.
 - the connections are at their **high-impedance state**

ROM Memory


- **Read-only memory** (ROM) permanently stores programs/data resident to the system.
 - and must not change when power disconnected
- Often called **nonvolatile memory**, because its contents *do not* change even if power is disconnected.
- programmed during fabrication at the factory

- The EPROM (**e**rasable **p**rogrammable **r**ead-**o**nly **m**emory) is commonly used when software must be changed often.
 - or when low demand makes ROM uneconomical
 - for ROM to be practical at least 10,000 devices must be sold to recoup factory charges
- An EPROM is programmed in the field on a device called an EPROM programmer.
- Also erasable if exposed to high-intensity ultraviolet light.
 - depending on the type of EPROM

- PROM memory devices are also available, although they are not as common today.
- The PROM (**programmable read-only memory**) is also programmed in the field by burning open tiny Ni-chrome or silicon oxide fuses.
- Once it is programmed, it cannot be erased.

- A newer type of **read-mostly memory** (RMM) is called the **flash memory**.
 - also often called an EEPROM (**e**lectrically **e**rasable **p**rogrammable **ROM**)
 - EAROM (**e**lectrically **a**lterable **ROM**)
 - or a NOVRAM (**n**onvolatile **RAM**)
- Electrically erasable in the system, but they **require more time** to erase than normal RAM.
- The **flash memory** device is used to store **setup information** for systems such as the video card in the computer.

Figure 10–2 The pin-out of the 2716, 2K × 8 EPROM. (Courtesy of Intel Corporation.)

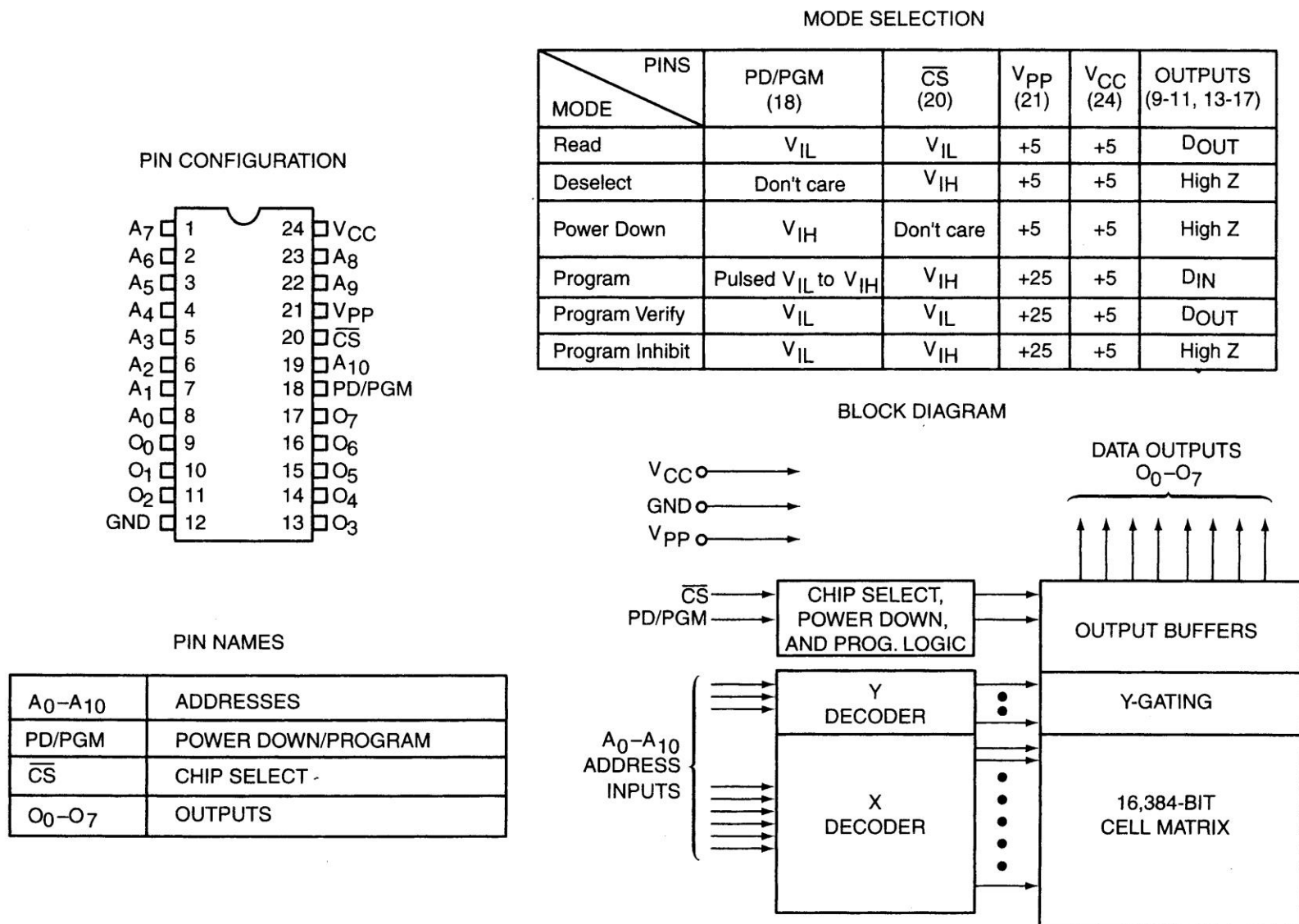


Static RAM (SRAM) Devices

- Static RAM memory devices retain data for as long as DC power is applied.
- Because no special action is required to retain data, these devices are called **static memory**.
 - also called **volatile memory** because they will not retain data without power
- The main difference between ROM and RAM is that RAM is written under normal operation, whereas ROM is programmed outside the computer and normally is **only read**.

Figure 10–4 The pin-out of the TMS4016, 2K × 8 static RAM (SRAM). (Courtesy of Texas Instruments Incorporated.)


**TMS4016 . . . NL PACKAGE
(TOP VIEW)**

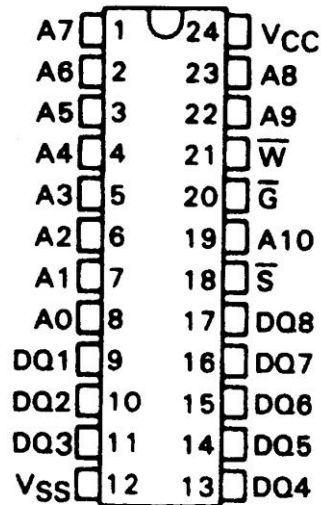

- SRAM is used when the size of the read/write memory is relatively small
- Today?, a small memory is less than 1M byte

PIN NOMENCLATURE	
A0 – A10	Addresses
DQ1 – DQ8	Data In/Data Out
\bar{G}	Output Enable
\bar{S}	Chip Select
VCC	+ 5-V Supply
VSS	Ground
\bar{W}	Write Enable

Figure 10–6 Pin diagram of the 62256, 32K × 8 static RAM.

 

PIN FUNCTION

$A_0 - A_{14}$	Addresses
$IO_0 - IO_7$	Data connections
\overline{CS}	Chip select
\overline{OE}	Output enable
\overline{WE}	Write enable
V_{CC}	+5V Supply
GND	Ground


Dynamic RAM (DRAM) Memory

- Available up to $256\text{M} \times 8$ (**2G bits**).
- DRAM is essentially the same as SRAM, except that it retains data for only 2 or 4 ms on an integrated capacitor.
- After 2 or 4 ms, the contents of the DRAM must be completely **rewritten** (*refreshed*).
 - because the capacitors, which store a logic 1 or logic 0, lose their charges

- In DRAM, the entire contents are refreshed with 256 reads in a 2- or 4-ms interval.
 - also occurs during a write, a read, or during a special refresh cycle
- DRAM requires so many address pins that manufacturers multiplexed address inputs.
- Figure 10–7 illustrates a $64K \times 4$ DRAM, the TMS4464, which stores 256K bits of data.
 - note it contains only eight address inputs where it should contain **16**—the number required to address **64K** memory locations

Figure 10–7 The pin-out of the TMS4464, 64K × 4 dynamic RAM (DRAM). (Courtesy of Texas Instruments Incorporated.)

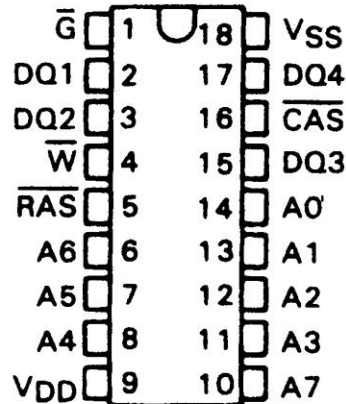**TMS4464 . . . JL OR NL PACKAGE
(TOP VIEW)**



(a)

PIN NOMENCLATURE	
A0-A7	Address Inputs
$\overline{\text{CAS}}$	Column Address Strobe
DQ1-DQ4	Data-In/Data-Out
$\overline{\text{G}}$	Output Enable
$\overline{\text{RAS}}$	Row Address Strobe
V _{DD}	+ 5-V Supply
V _{SS}	Ground
$\overline{\text{W}}$	Write Enable

(b)

- 16 address bits can be forced into eight address pins in two 8-bit increments
- this requires two special pins: the **column address strobe** ($\overline{\text{CAS}}$) and **row address strobe** ($\overline{\text{RAS}}$)

- First, A_0 – A_7 are placed on the address pins and **strobed into** an internal **row latch** by \overline{RAS} as the row address.
- Next, address bits A_8 – A_{15} are placed on the same eight address inputs and **strobed into** an internal **column latch** by \overline{CAS} as the column address
- The 16-bit address in the internal latches addresses the contents of one of the 4-bit **memory locations**.
 - \overline{CAS} also performs chip selection input to DRAM

Figure 10–8 RAS, CAS and address input timing for the TMS4464 DRAM.
(Courtesy of Texas Instruments Incorporated.)



 


Figure 10–9 Address multiplexer for the TMS4464 DRAM.

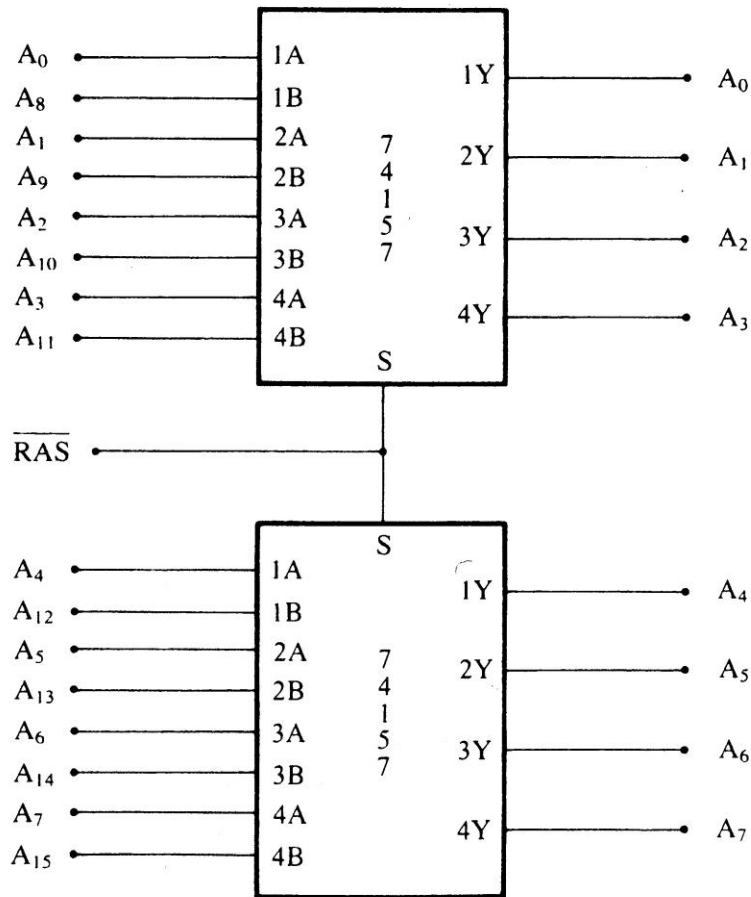

- multiplexers used to strobe column and row addresses into the address pins on a pair of TMS4464 DRAMs.
- the $\overline{\text{RAS}}$ signal not only strobes the row address into the DRAMs, but it also selects which part of the address is applied to the address inputs.

Figure 10–10 The 41256 dynamic RAM organized as a 256K × 1 memory device.

 

PIN FUNCTIONS

A ₀ - A ₈	Addresses
Din	Data in
Dout	Data out
$\overline{\text{CAS}}$	Column Address Strobe
$\overline{\text{RAS}}$	Row Address Strobe
$\overline{\text{WR}}$	Write enable
V _{CC}	+5V Supply
GND	Ground

- the pin-out of the 41256 dynamic RAM
- this device is organized as a 256K × 1 memory
- requires as little as 70 ns to access data

10–2 ADDRESS DECODING

- In order to attach a memory device to the microprocessor, it is necessary to **decode** the address sent from the microprocessor.
- Decoding makes the memory function at a unique section or partition of the memory map.
- Without an address decoder, only one memory device can be connected to a microprocessor, which would make it virtually useless.


Why Decode Memory?

- The 8088 has **20** address connections and the 2716 EPROM has **11** connections.
- The 8088 sends out a **20**-bit memory address whenever it reads or writes data.
 - because the 2716 has only **11** address pins, there is a mismatch that must be corrected
- The decoder corrects the **mismatch** by decoding address pins that do not connect to the memory component.

Simple NAND Gate Decoder


- When the $2K \times 8$ EPROM is used, address connections $A_{10}-A_0$ of 8088 are connected to address inputs $A_{10}-A_0$ of the EPROM.
 - the remaining nine address pins ($A_{19}-A_{11}$) are connected to a NAND gate decoder
- The **decoder** selects the EPROM from one of the 2K-byte sections of the 1M-byte memory system in the 8088 microprocessor.
- In this circuit a NAND gate decodes the memory address, as seen in Figure 10-13.

Figure 10–13 A simple NAND gate decoder that selects a 2716 EPROM for memory location FF800H–FFFFFFH.

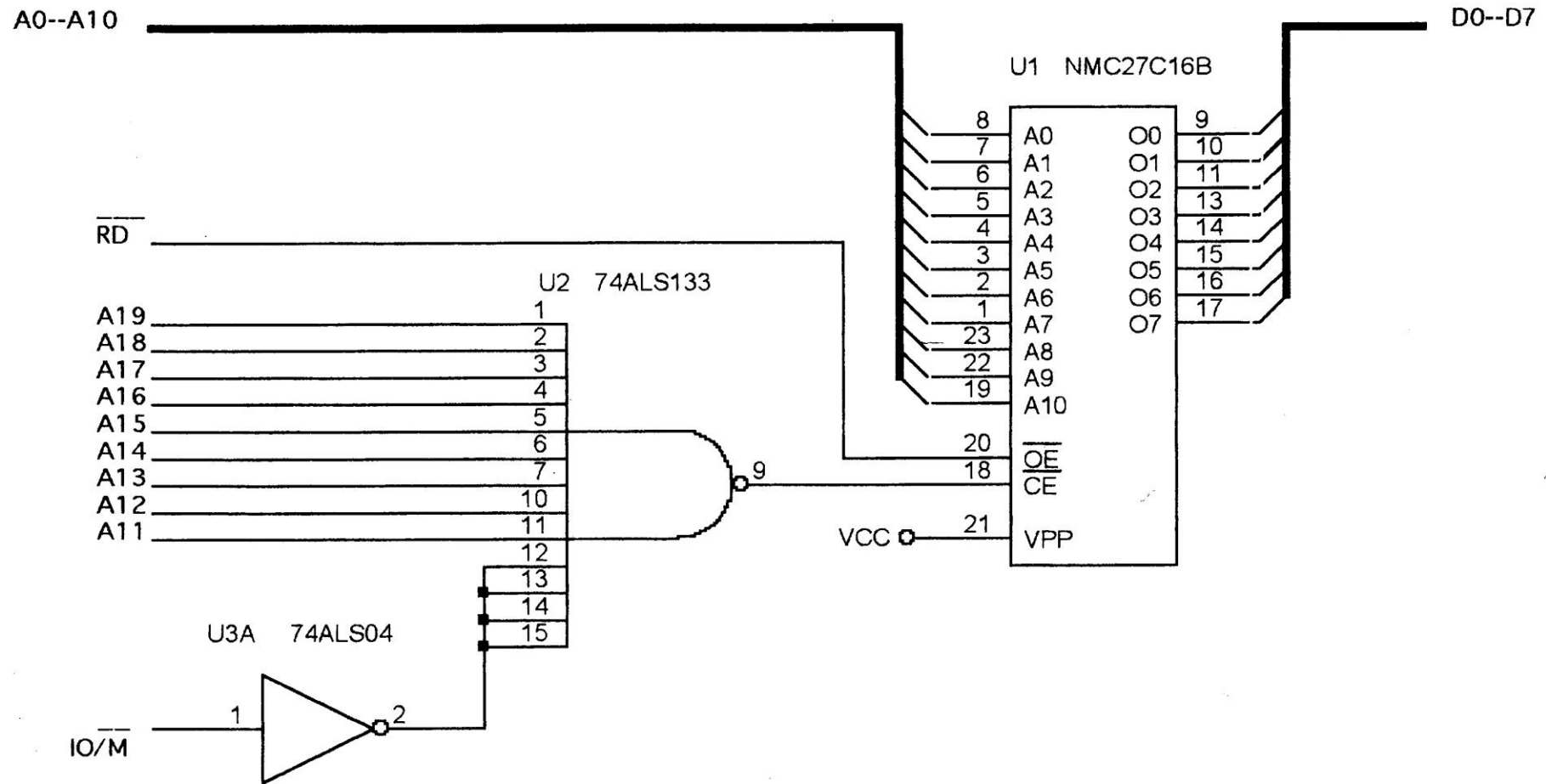

- If the 20-bit binary address, decoded by the NAND gate, is written so that the leftmost nine bits are 1s and the rightmost 11 bits are **don't cares** (X), the actual address range of the EPROM can be determined.
 - a *don't care* is a logic 1 or a logic 0, whichever is appropriate
- Because of the excessive cost of the NAND gate decoder and inverters often required, this option requires an **alternate** be found.

The 3-to-8 Line Decoder (74LS138)

 

- a common integrated circuit decoder found in many systems is the 74LS138 3-to-8 line decoder.

Inputs						Outputs							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	0	1	1	1
0	0	1	1	0	1	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0


Figure 10–14 The 74LS138 3-to-8 line decoder and function table.

Sample Decoder Circuit


- The outputs of the decoder in Figure 10–15, are connected to eight different 2764 EPROM memory devices.
- The decoder selects eight 8K-byte blocks of memory for a total capacity of 64K bytes.
- This figure also illustrates the address range of each memory device and the common connections to the memory devices.

Figure 10–15 A circuit that uses eight 2764 EPROMs for a 64K × 8 section of memory in an 8088 microprocessor-based system. The addresses **selected** in this circuit are F0000H–FFFFFH.

 - decoder's outputs are connected to the \overline{CE} of the EPROMs,
- \overline{RD} signal from 8088 is connected to the OE of the EPROMs



MEMORY INTERFACE

 


- In this circuit, a **three-input** NAND gate is connected to address bits A_{19} – A_{17} .
- When all three address inputs are high, the output of this NAND gate goes low and enables input $\overline{G2B}$ of the 74LS138.
- Input G1 is connected directly to A_{16} .
- In order to enable this decoder, the first four address connections (A_{19} – A_{16}) must all be high.

- Address inputs C, B, and A connect to microprocessor address pins A_{15} – A_{13} .
- These **three** address inputs determine which output pin goes low and which EPROM is selected whenever 8088 outputs a memory address within this **range** to the memory system.

The Dual 2-to-4 Line Decoder (74LS139)


- Figure 10–16 illustrates both the pin-out and the truth table for the 74LS139 **dual** 2-to-4 line decoder.
- 74LS139 contains **two** separate 2-to-4 line decoders—each with its own address, enable, and output connections.
- A more complicated decoder using the 74LS139 decoder appears in Figure 10–17.

Figure 10–16 The pin-out and truth table of the 74LS139, **dual** 2-to-4 line decoder.

 

Inputs			Outputs			
\overline{E}	A	B	$\overline{Y_0}$	$\overline{Y_1}$	$\overline{Y_2}$	$\overline{Y_3}$
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

Figure 10–17 A sample memory system constructed with a 74HCT139.

 

PLD Programmable Decoders


- Three SPLD (**s**imple **PLD**) devices function in the same manner but have **different names**:
 - PLA (**p**rogrammable **l**ogic **a**rray)
 - PAL (**p**rogrammable **a**rray **l**ogic)
 - GAL (**g**ated **a**rray **l**ogic)
- In existence since the mid-70s, they have appeared in memory system and digital designs since the early 1990s.

- PAL and PLA are fuse-programmed, and some PLD devices are erasable devices.
 - all are arrays of programmable logic elements
- Other PLDs available:
 - CPLDs (**c**omplex **p**rogrammable **l**ogic **d**evices)
 - FPGAs (**f**ield **p**rogrammable **g**ate **a**rrays)
 - FPICs (**f**ield **p**rogrammable **i**nter**c**onnect)
- These PLDs are more complex than the SPLDs used more commonly in designing a complete system.


Combinatorial Programmable Logic Arrays

- Fig 10–18 shows the internal structure of a PAL16L8 constructed with AND/OR gate logic.
- It has 10 fixed inputs, two fixed outputs, and six pins **programmable** as inputs or outputs.
- Programming is accomplished by blowing fuses to connect inputs to the OR gate array.
- It is ideal as a **decoder** because of its structure, also because outputs are active low.

Figure 10–18 The PAL16L8. (Copyright Advanced Micro Devices, Inc., 1988. Reprinted with permission of copyright owner. All rights reserved.)

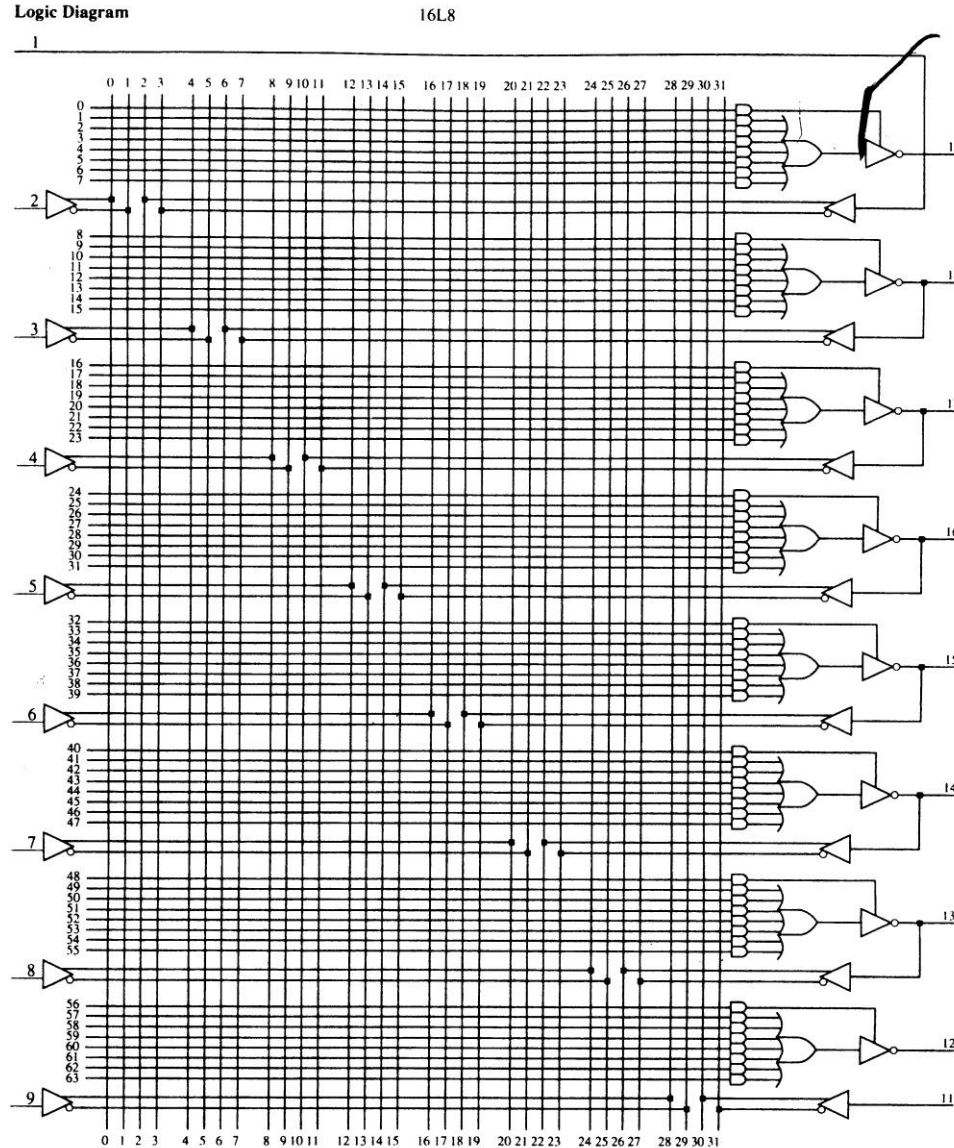

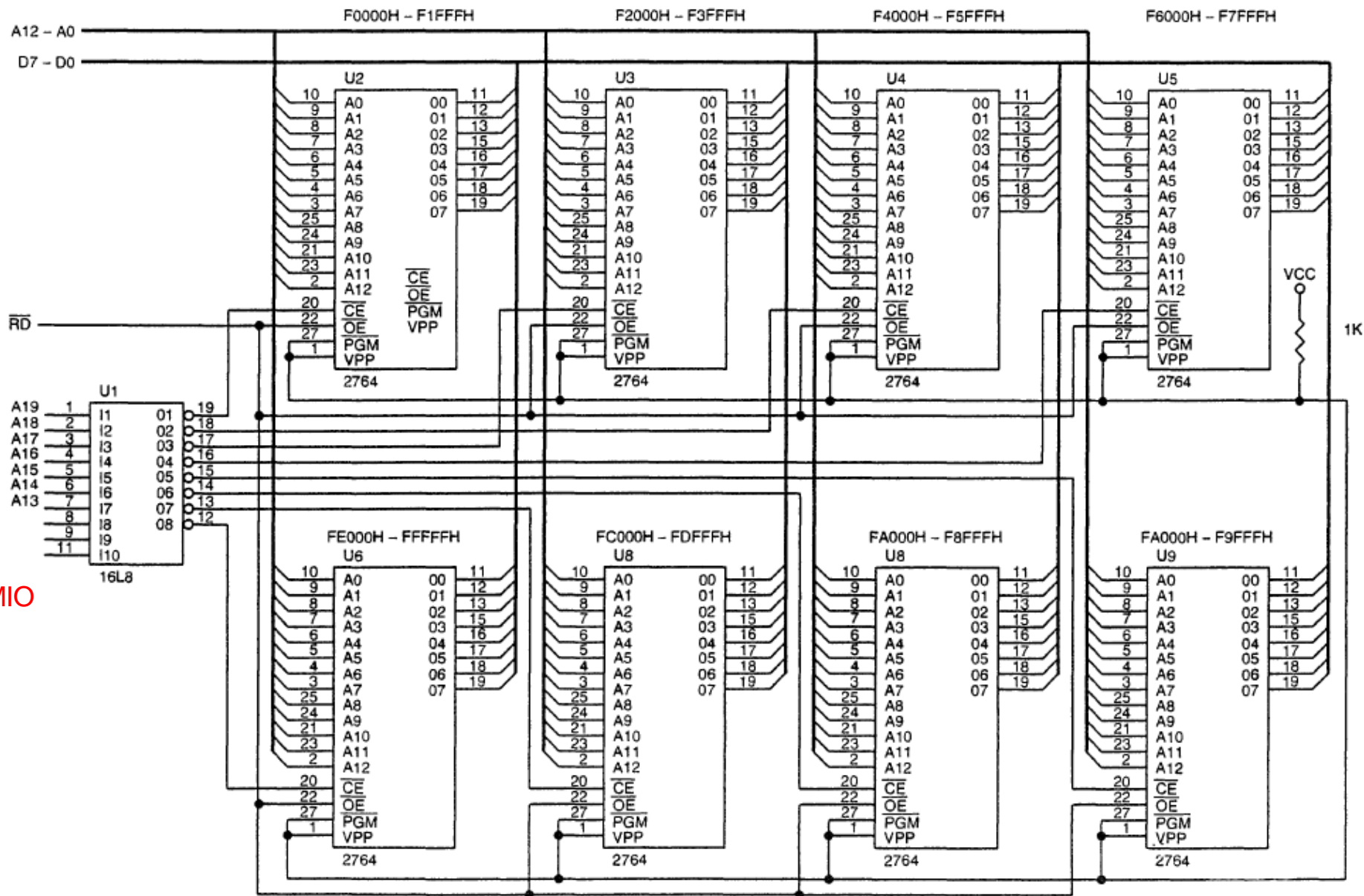- A PAL is programmed with software such as PALASM, the PAL assembler program.
- PLD design is accomplished using HDL (**hardware description language**) or VHDL (**verilog HDL**).
 - VHDL and its syntax are currently the industry standard for programming PLD devices
- Various editors attempt to ease the task of defining the pins.
 - the authors believe it is easier to use NotePad



CHIP DECODER1 PAL16L8

;pins 1 2 3 4 5 6 7 8 9 10
 A19 A18 A17 A16 A15 A14 A13 NC NC GND

;pins 11 12 13 14 15 16 17 18 19 20
 NC O8 O7 O6 O5 O4 O3 O2 O1 VCC

EQUATIONS

/O1 = A19 * A18 * A17 * A16 * /A15 * /A14 * /A13

/O2 = A19 * A18 * A17 * A16 * /A15 * /A14 * A13

/O3 = A19 * A18 * A17 * A16 * /A15 * A14 * /A13

/O4 = A19 * A18 * A17 * A16 * /A15 * /A14 * A13 /A15 *A14*A13

/O5 = A19 * A18 * A17 * A16 * A15 * /A14 * /A13

/O6 = A19 * A18 * A17 * A16 * A15 * A14 * A13


/O7 = A19 * A18 * A17 * A16 * A15 * /A14 * /A13

/O8 = A19 * A18 * A17 * A16 * A15 * /A14 * A13

Interfacing EPROM to the 8088

- Fig 10–20 shows an 8088/80188 connected to three 27256 EPROMs, $32\text{K} \times 8$ devices.
 - 74HCT138 decoder in this illustration decodes **three** $32\text{K} \times 8$ blocks of memory for a total of $96\text{K} \times 8$ bits of physical address space for 8088/80188
- The decoder is selected for an address range that begins at E8000H and continues through location FFFFFFFH—the upper 96K bytes of memory.

Figure 10–20 Three 27256 EPROMs interfaced to the 8088 microprocessor.

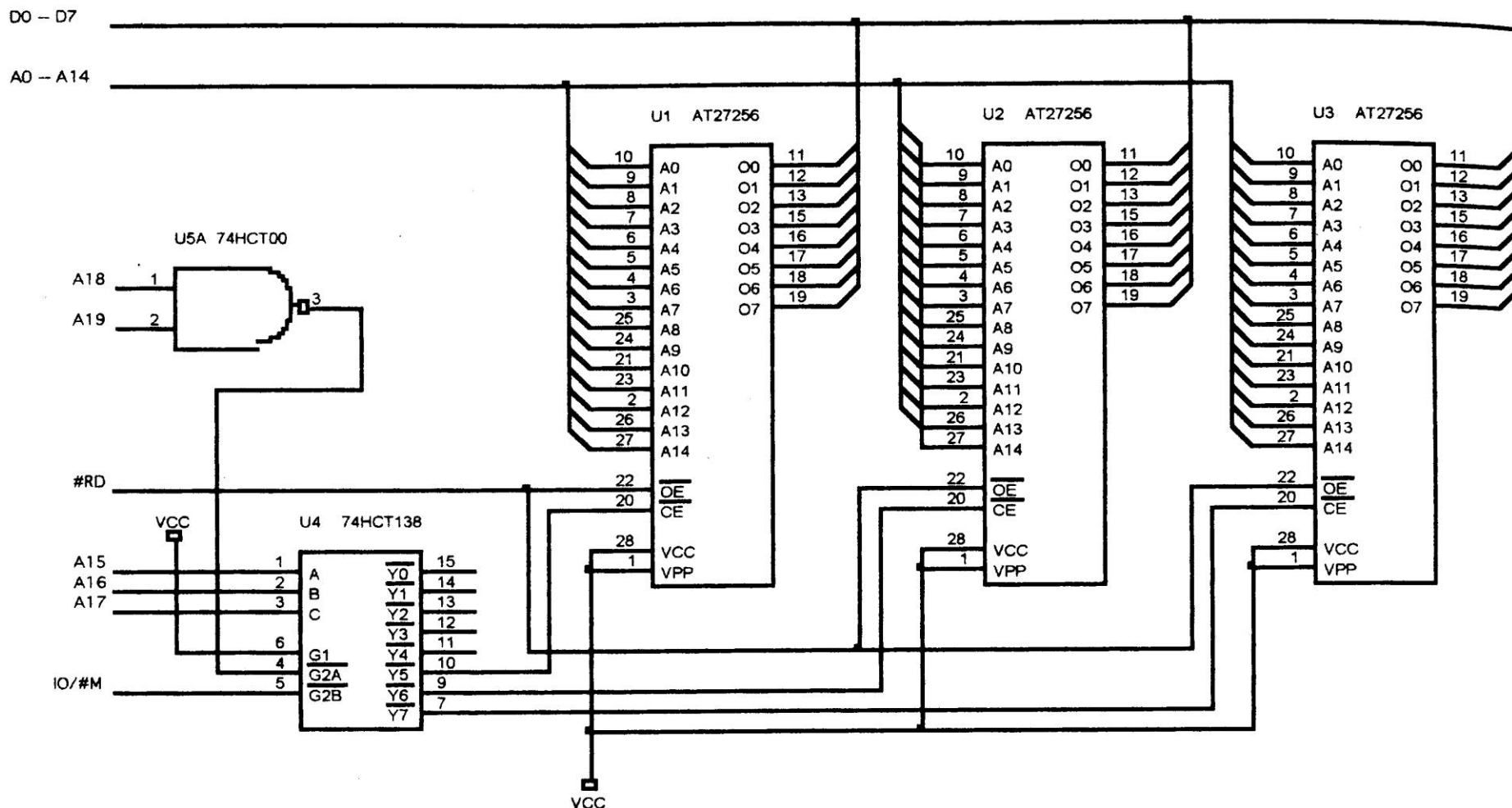


- This section of memory is an EPROM because **FFFF0H** is where the 8088 starts **to** execute instructions after a hardware reset.
 - often called the **cold-start location**
- The software stored in this section of memory would contain a **JMP** instruction at location **FFFF0H** that jumps to location **E8000H**
 - so the remainder of the program can execute
- In this circuit, U_1 is decoded at addresses E8000H–EFFFFH, U_2 is decoded at F0000H–F7FFFH, and U_3 at F8000H–FFFFFFH.

Interfacing RAM to the 8088

- RAM is easier to interface than EPROM as most RAM does not require **wait states**.
 - ideal section of memory for RAM is the very bottom, which contains vectors for interrupts
- **Interrupt vectors** are often modified by software packages,
 - it is important to encode this section of the memory with RAM
- Fig 10–21 shows sixteen 62256 static RAMs interfaced to the 8088, beginning at 00000H.



Figure 10–21 A 512K-byte static memory system using 16 62256 SRAMs.

 

- this board uses **two** decoders to select **16** RAM components, and a third to select other decoders for the appropriate memory sections
- **sixteen** 32K RAMs fill memory from 00000H through 7FFFFH, for 512K bytes memory.

16-Bit Bus Control

- The data bus of 8086, 80186, 80286, and 80386SX is twice as the 8088/80188.
 - processors must be able to write data to any 16-bit location—or any 8-bit location
- The 16-bit data bus is divided into 2 **sections** (or **banks**) 8 bits wide so the processor can write to either half (8-bit) or both halves (16-bit).
 - one bank (**low bank**) holds all even-numbered memory locations
 - the other bank (**high bank**) holds all the odd-numbered memory locations

  


Note: A_0 is labeled $\overline{\text{BLE}}$ (Bus low enable) on the 80386SX.

- Bank selection is accomplished in two ways:
 1. separate write signal is developed to select a write to each bank of the memory
 2. separate decoders are used for each bank
- The first technique is by far the least costly approach to **memory interface**.
- The second technique is only used in a system that must achieve the **most efficient** use of the power supply.

Separate Bank Decoders

- **Separate bank** decoders is often the least effective way to decode memory addresses for the 8086, 80186, 80286, and 80386SX.
- This method is sometimes used, but it is difficult to understand why in most cases.
 - one reason may be to conserve energy, as only banks selected are enabled
- Fig 10–28 shows two 74LS138s used to select 64K RAM memory components for the 80386SX microprocessor (**24-bit address**).

Figure 10–28 Separate bank decoders.

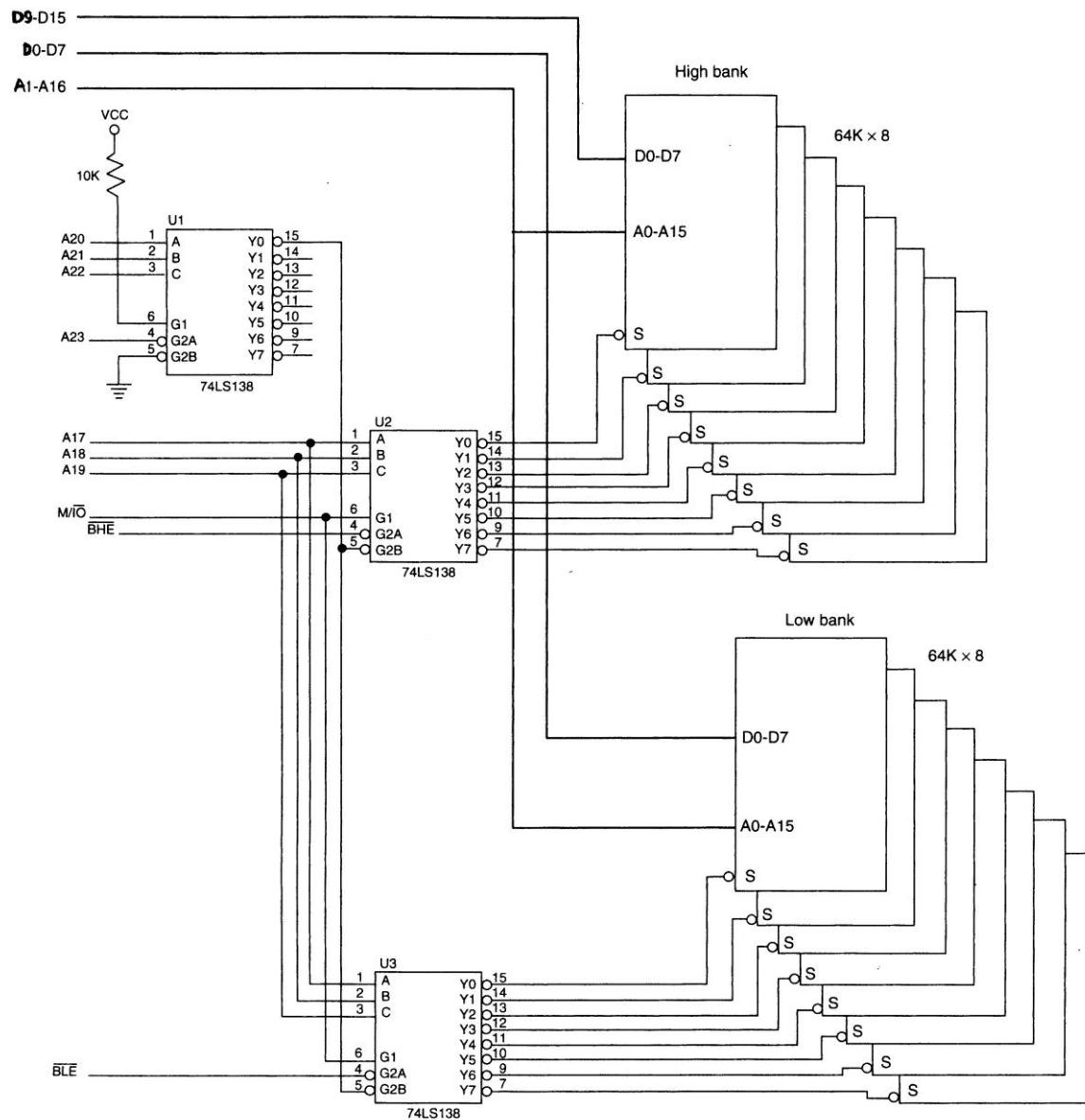

The I


Pentium Pro Processor, Pentium II, Pentium, 4, and Core2 with 64-bit Extensions
Architecture, Programming, and Interfacing, Eighth Edition
Barry B. Brey

Copyright ©2009 by Pearson Education, Inc.
Upper Saddle River, New Jersey 07458 • All rights reserved.

Separate Bank Write Strobes


- The effective way to handle **bank selection** is a separate write **strobe** for each bank.
 - this requires only one decoder to select a 16-bit-wide memory, which saves money
- Fig 10–29 depicts generation of separate 8086 **write strobes**.
- Separate read strobes for each bank are usually unnecessary because 8086 through 80386SX read only the byte of data they need at any given time from half of the data bus.

Figure 10–29 The memory bank write selection input signals: $\overline{\text{HWR}}$ (high bank write) and $\overline{\text{LWR}}$ (low bank write).

 


- a memory system that uses separate write strobes is constructed differently from the 8088 or the system using separate memory banks
- memory in a system using separate write strobes is decoded as 16-bit-wide

Figure 10–30 A 16-bit-wide memory interfaced at memory locations 06000H–06FFFH.

 


- the program for the GAL22V10 decoder is illustrated in Example 10–7
- notice that not only is the memory selected, but both the lower and upper write strobes are also generated by the PLD
- a GAL22V10 to both decode memory and generate the separate write strobe

Figure 10–31 A memory system for the 8086 that contains a 64K-byte EPROM and a 128K-byte SRAM.

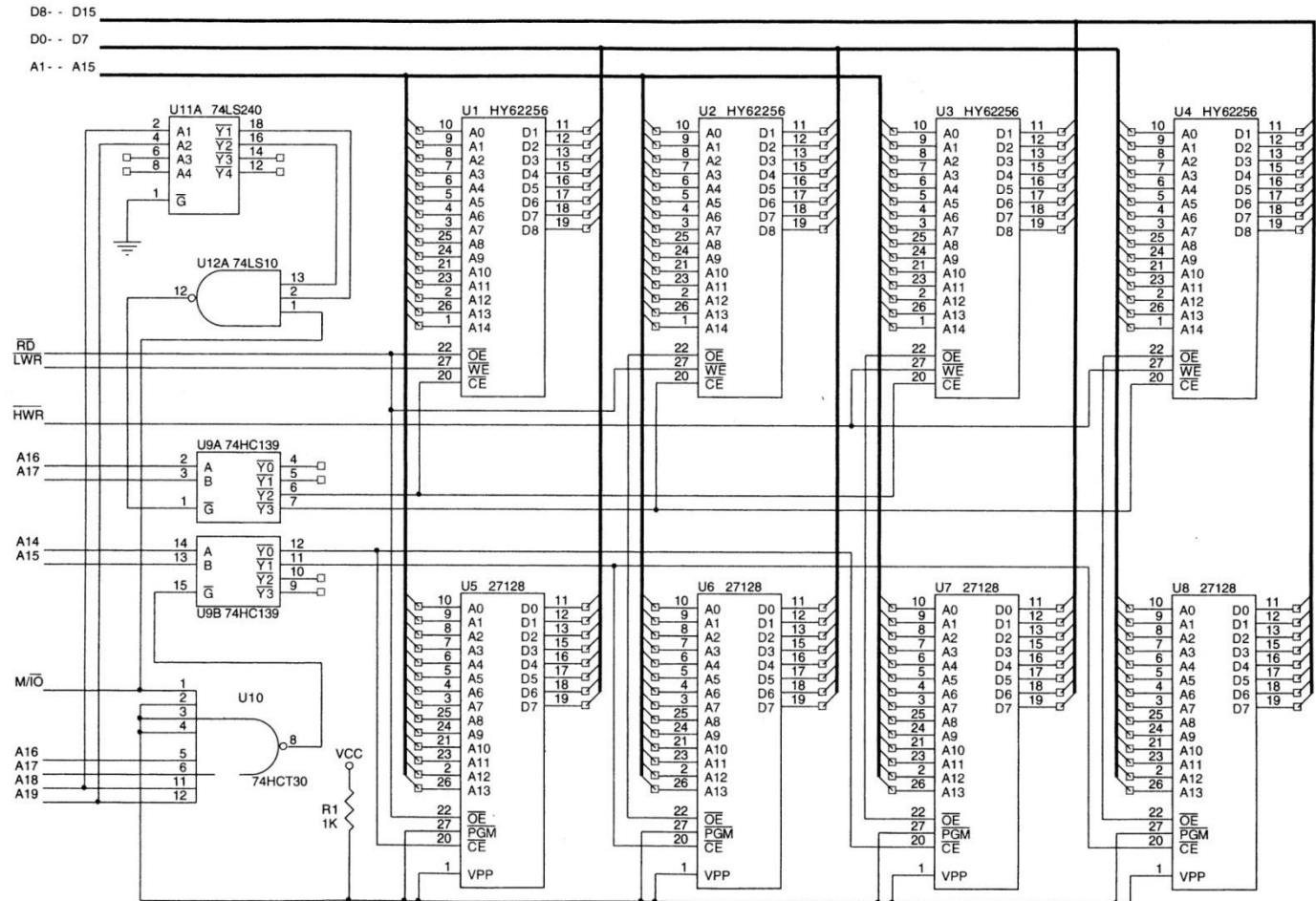


 - four 27128 EPROMs compose a 32K × 16-bit memory at F0000–FFFFFFH and four 62256 that compose 64K × 16-bit at 00000H–1FFFFH
- though 16 bits wide, it is still numbered in bytes



- Fig 10–32 shows a memory connected to an 80386SX by using a GAL22V10 as a decoder.
- This interface contains 256K bytes of EPROM in the form of four 27⁵¹² (64K × 8) EPROMs and 128K bytes of SRAM memory found in four 62²⁵⁶ (32K × 8) SRAMs.
- The PLD decodes the 16-bit-wide memory addresses at locations 000000H–01FFFFH for the SRAM and locations FC0000H–FFFFFFH for the EPROM.

Figure 10–32 An 80386SX memory system containing 256K of EPROM and 128K of SRAM.

 

10–5 80386DX and 80486 (32-Bit) MEMORY INTERFACE

- A 32-bit memory system has a 32-bit data bus and **four banks** of memory.
- Both 80386DX and 80486 (SX and DX) contain a **32-bit address bus** that usually requires PLD decoders instead of integrated decoders.
 - because of the **sizable number** of address bits

Memory Banks


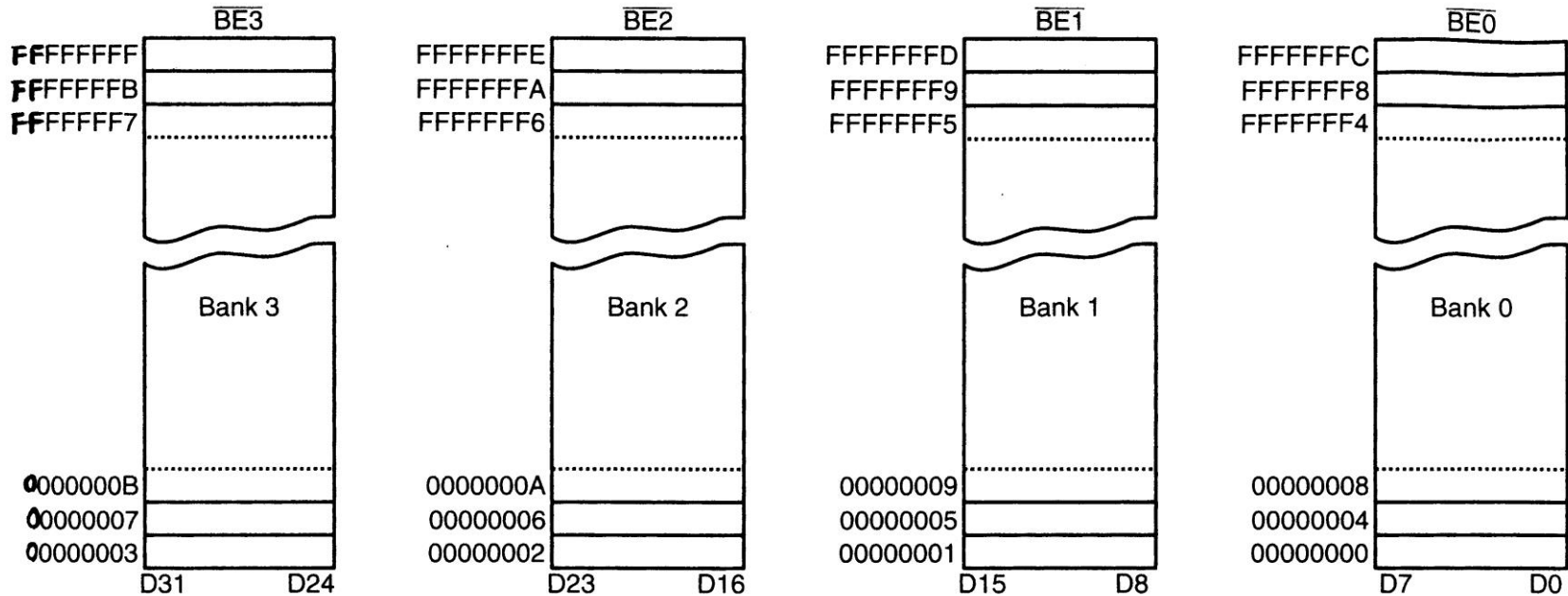


Figure 10–33 Memory organization for the 80386DX and 80486 microprocessors.

- these large memory systems contain four 8-bit-wide banks that contain up to 1G byte each.
- bank selection is accomplished by bank selection signals BE3, BE2, BE1 and BE0
- if a 32-bit number is transferred, all four banks are selected; if a 16-bit number, two banks; if 8 bits a single bank is selected.

Figure 10–34 Bank write signals for the 80386DX and 80486 microprocessors.

 


- separate write strobes are developed, by using a simple OR gate or other logic component

32-Bit Memory Interface

- A memory interface for 80386DX or 80486 requires **four bank write strobes** and decoding a 32-bit address.
 - there are no integrated decoders, such as the 74LS138, that can easily accommodate a memory interface for the 80386DX or 80486
- Figure 10–35 shows a $512\text{K} \times 8$ SRAM memory system for the 80486.
 - This uses **eight** $64\text{K} \times 8$ SRAM memory devices, a PLD, and an OR gate

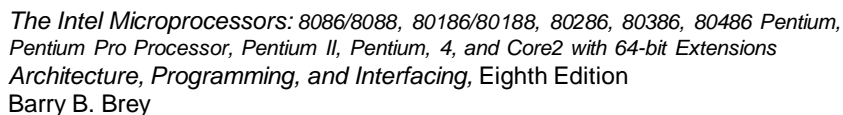Which addresses can be put instead of A20




- 80386DX and 80486 microprocessors operate with very **high** clock rates.
 - usually require **wait states** for memory access
- The interface provides a signal used with the **wait state generator**.
- Other devices with these higher speed microprocessors are cache memory and interleaved memory systems.

10–6 PENTIUM THROUGH CORE2 (64-Bit) MEMORY INTERFACE

- The Pentium - Core2 contain a **64-bit data bus**, which requires **eight decoders** (one per bank) or **eight separate** write signals.
 - except the P24T version of the Pentium
- In most systems, **separate** write signals are used when interfacing memory.
- Figure 10–36 shows the Pentium memory organization and its **eight memory banks**.

Figure 10–36 The memory organization of the Pentium–Core2 microprocessors.

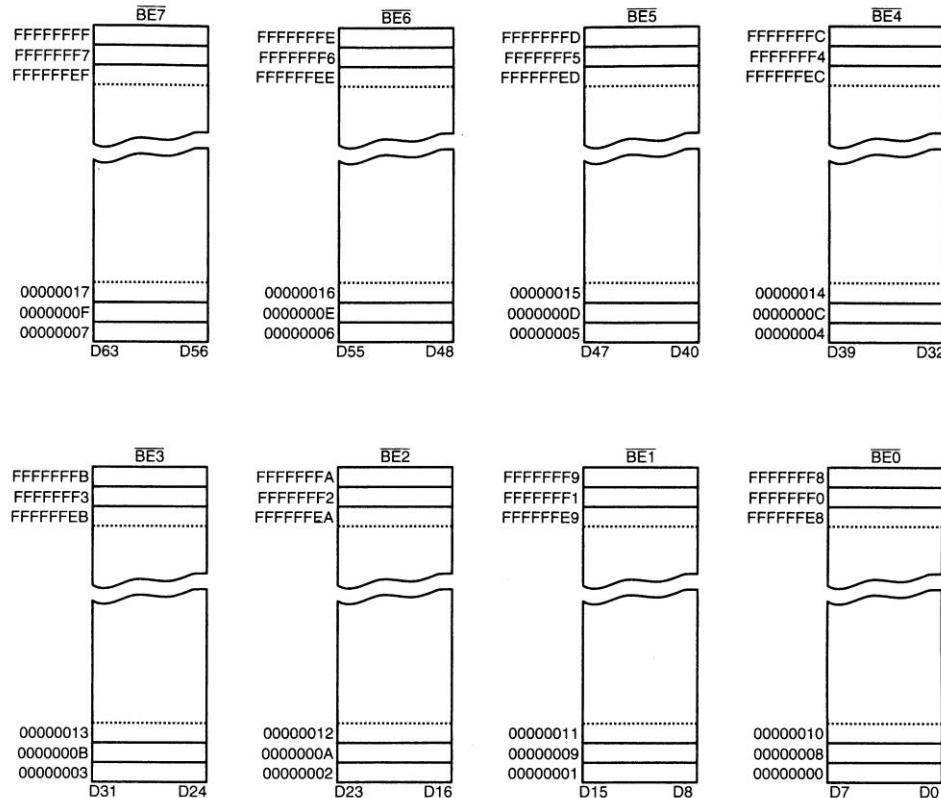


- this is almost identical to 80486, except it contains eight banks instead of four
- as with earlier versions, this organization is required for upward compatibility

Figure 10–37 A small 512K-byte EPROM memory interfaced to the Pentium–Core2 microprocessors.

- separate write strobe signals are obtained by combining bank enable signals with the MWTC signal, generated by combining the M/IO with W/R
- the circuit employed for bank write signals is shown here
- a PLD is often used for bank write signal generation

Figure 10–37 A small 512K-byte EPROM memory interfaced to the Pentium–Core2 microprocessors.

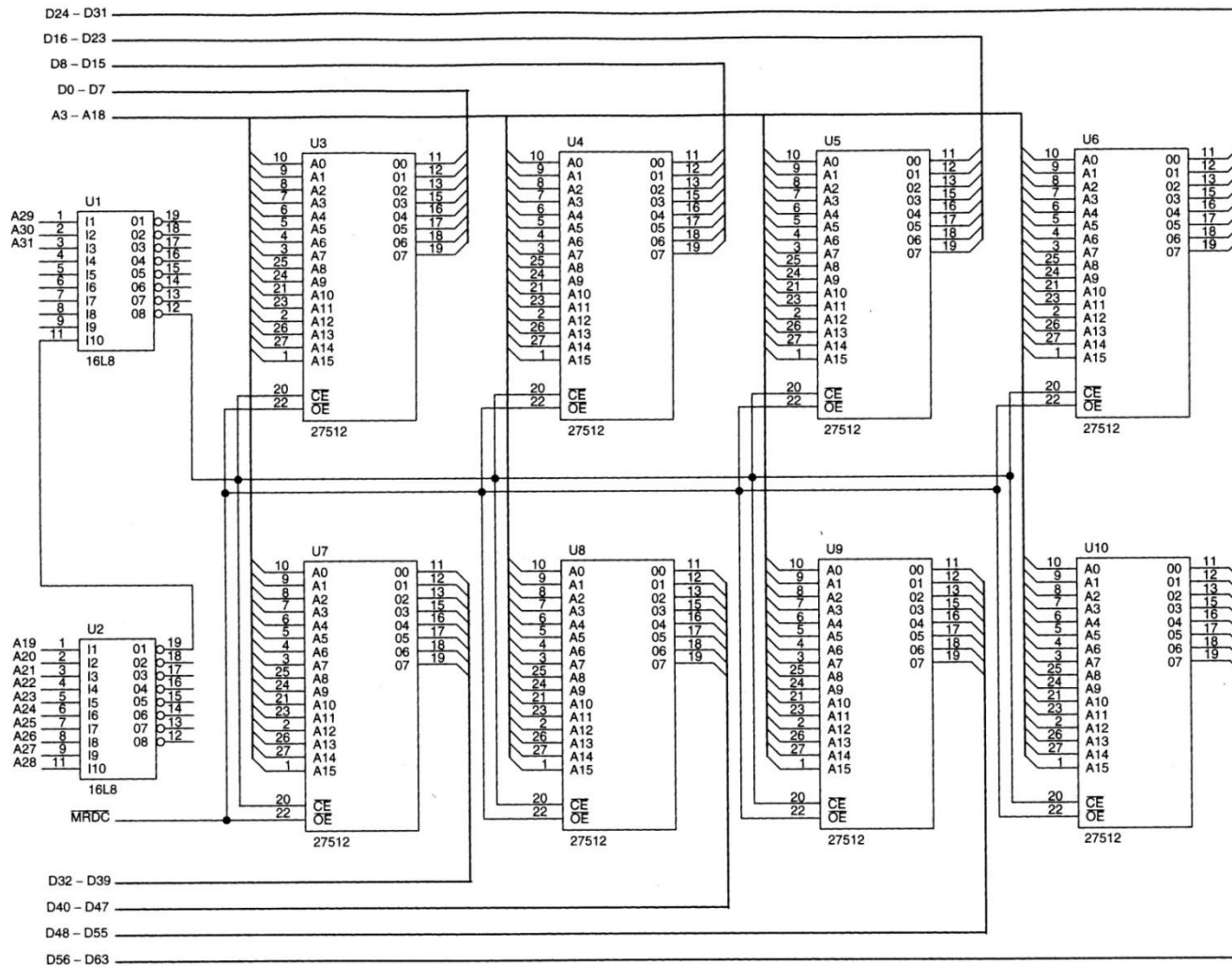


64-Bit Memory Interface

- this system contains eight 27C4001 EPROM (512K × 8), at FFC00000H through FFFFFFFFH
- total memory size of 4M bytes organized so each bank contains two memory components

Figure 10–38 A small 4M-byte EPROM memory system for the Pentium–Core2 microprocessors.

FIGURE 10-38 A small 4M-byte EPROM memory system for the Pentium-Core2 microprocessors.

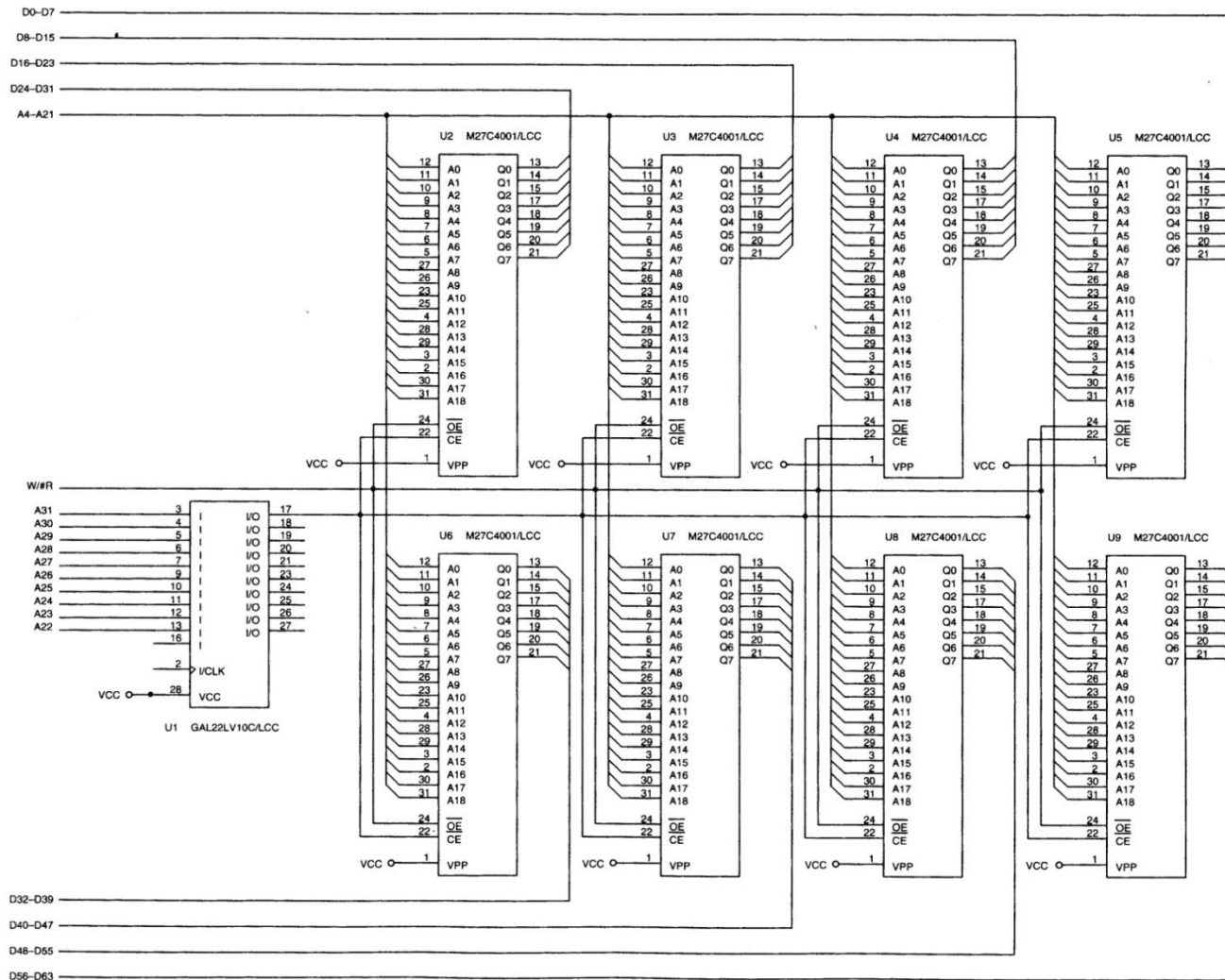

10–7 DYNAMIC RAM

- Because RAM is often large, it requires many SRAMs at great cost or a few DRAMs (**dynamic RAMs**) at much reduced cost.
- IC manufacturers have provided a dynamic RAM controller with address multiplexers and timing circuitry necessary for refreshing.
- This section of the text covers the DRAM and provides information on the use of a dynamic controller in a memory system.

DRAM Revisited

- DRAM must be refreshed periodically as it stores data internally on capacitors that lose charge in a short period of time.
 - to refresh DRAM, contents of a section of the memory must periodically be **read** or **written**
- Any read or write automatically refreshes an entire section of the DRAM.
- The number of bits refreshed depends on the size of the memory component and its internal organization.

- Refresh cycles are done with a read, write, or a special refresh that doesn't read or write.
- The refresh cycle is internal to the DRAM and often accomplished while other memory components in the system operate.
 - this is called *hidden refresh*, *transparent refresh*, or sometimes, *cycle stealing*
- To do a hidden refresh while other memory components are *functioning*, an $\overline{\text{RAS}}$ -only cycle strobes a row address into the DRAM to select a row of bits to be refreshed.

- The $\overline{\text{RAS}}$ input also causes the selected row to be read and rewritten into the selected bits.
 - this recharges internal capacitors that store data
- This refresh is **hidden** from the system because it occurs while the processor is **reading** or **writing other sections** of memory

Figure 10–39 The internal structure of a 256K × 1 DRAM. Note that each of the internal 256 words are 1024 bits wide.

electrical characteristics over recommended operating free air temperature range (unless otherwise noted)

PARAMETER		TEST CONDITIONS		MIN	TYP	MAX	UNIT
V_{DD}	Supply voltage	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			1.5 1.2	V
I_{DD}	Supply current	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			100 100	μA
t_{RD}	Read access time	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			15 15	ns
t_{WR}	Write access time	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			15 15	ns
t_{RCD}	Row to column delay	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			15 15	ns
t_{RC}	Row cycle time	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			15 15	ns
t_{RAS}	Row address strobe pulse width	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			15 15	ns
t_{CAS}	Column address strobe pulse width	$V_{DD} = 1.5$ $V_{DD} = 1.2$	$T_A = 0^\circ\text{C}$ $T_A = 75^\circ\text{C}$			15 15	ns

timing requirements over recommended supply voltage range and operating free air temperature range

PARAMETER	1.5V MAX		1.2V MAX		TYPICAL		UNIT
	MIN	MAX	MIN	MAX	MIN	MAX	
t_{RD}	15	15	15	15	15	15	ns
t_{WR}	15	15	15	15	15	15	ns
t_{RCD}	15	15	15	15	15	15	ns
t_{RC}	15	15	15	15	15	15	ns
t_{RAS}	15	15	15	15	15	15	ns
t_{CAS}	15	15	15	15	15	15	ns

switching characteristics over recommended voltage range, $T_A = 0^\circ\text{C}$ to 75°C


PARAMETER	1.5V MAX		1.2V MAX		TYPICAL		UNIT
	MIN	MAX	MIN	MAX	MIN	MAX	
t_{RD}	15	15	15	15	15	15	ns
t_{WR}	15	15	15	15	15	15	ns
t_{RCD}	15	15	15	15	15	15	ns
t_{RC}	15	15	15	15	15	15	ns
t_{RAS}	15	15	15	15	15	15	ns
t_{CAS}	15	15	15	15	15	15	ns

- DRAM internal organization has a series of rows and columns
- a 256K × 1 DRAM has 256 columns, each containing 256 bits, or rows organized into **four sections** of 64K bits
- When memory is addressed, the column address selects a column (or internal memory word) of 1024 bits


Figure 10–40 The timing diagram of the $\overline{\text{RAS}}$ refresh cycle for the TMS4464 DRAM. (Courtesy of Texas Instruments Corporation.)

- the difference between the $\overline{\text{RAS}}$ and a read or write is that it applies only a refresh address, usually obtained from a 7- or 8-bit binary counter.
- counter size is determined by type of DRAM being refreshed
- refresh counter is incremented at the end of each refresh cycle
- all rows are refreshed in 2 or 4 ms, depending on the DRAM

 
Timing waveform of read cycle (10 ns, 100 ns)



 Timing waveform of write cycle (10 ns, 100 ns)



 Timing waveform of write cycle (10 ns, 100 ns, 100 ns)



Timing waveform of write cycle (10 ns, 100 ns, 100 ns)

1. The refresh cycle is initiated by the $\overline{\text{RAS}}$ signal. The $\overline{\text{RAS}}$ signal is active (marked with an 'X') during the refresh operation. The $\overline{\text{RAS}}$ signal is a pulse that initiates the refresh. The DATA line shows the data being written to the memory. The diagram includes timing parameters such as t_{RAS} , t_{WD} , and $t_{\text{WD,STB}}$.

- If there are **256 rows** to be refreshed within 4 ms, the refresh cycle must be activated at least once every **15.6 μ s**.
 - in a modern system such as a 3.0 GHz Pentium 4, 15.6 μ s is a great deal of time
- Since the 3.0 GHz Pentium 4 executes an instruction in about one-third ns, it can execute about 46,000 instructions between refreshes.
- In new machines much **less than 1%** (**≈ 0.002 %**) is required for a refresh.

EDO Memory

- Slight modification to the DRAM changes it an EDO (**e**xtended **d**ata **o**utput) DRAM device.
- In EDO memory, any memory access, including a **refresh**, stores the 256 bits selected by $\overline{\text{RAS}}$ into latches.
- This slight modification increases system **performance** by about **15%** to **25%**.
- Although EDO memory is no longer available, the technique is employed in modern DRAM.

SDRAM

- Synchronous dynamic RAM (**SDRAM**) is used with **most newer systems** because of speed.
- Versions are available with access times as low as 7 ns, for the 133 MHz bus.
- When a burst transfer occurs to the SDRAM from the processor, it takes three or four bus clocks before the first 64-bit number is read.
- Each **subsequent number** is read without wait states and in one bus cycle each.

- Because SDRAM bursts read four 64-bit numbers, the second through fourth require **no waits**, and can be read in one bus cycle each, SDRAM outperforms standard DRAM .
- Most estimates place SDRAM at about a **10% performance increase over EDO** memory.

DDR

- Double-data rate (DDR) memory is the latest improvement in DRAM modifications.
 - DDR memory data at double SDRAM speed because it transfers on each edge of the clock
 - the positive edge is used for a transfer and so is the negative edge
- Even though this seems as if it doubles the speed of the memory, it really does not.
 - access time problems still exist, with even most advanced memory requiring access time of 40 ns.

DRAM Controllers

- In most systems, a DRAM controller-IC performs **address multiplexing** and generation of the DRAM **control signals**.
 - newer embedded processors, such as 80186/8, include refresh circuitry as part of the processor
- Most modern computers contain the DRAM controller **in the chip set** so a stand-alone DRAM controller is not available.

- The DRAM controller in the chip set for the microprocessor times refresh cycles and inserts refresh cycles into the timing.
- The memory refresh is transparent to the microprocessor, because it really does not control refreshing.
- For Pentium II, III, and P4, DRAM control is built in the chip set provided by Intel or AMD.
- In the future, even the chip set will undoubtedly be built into the microprocessor.

SUMMARY

- All memory devices have **address inputs**; data inputs and outputs, or just outputs; a pin for selection; and one or more pins that **control** the operation of the memory.
- Address connections on a memory component are used to select one of the memory locations within the device.
- **Ten address pins** have **1024 combinations** and therefore are able to address 1024 different memory locations.

SUMMARY

(*cont.*)

- Data connections on a memory are used to enter information to be stored in a memory location and also to retrieve information read from a memory location.
- Manufacturers list their memory as, for example, 4K x 4, which means that the device has 4K memory locations (4096) and that four bits are stored in each location.

SUMMARY

(*cont.*)

- An EPROM memory is programmed by an EPROM programmer and can be erased if exposed to ultraviolet light.
- Today, EPROMs are available in sizes from 1K x 8 up to **512K x 8** and larger.
- The flash memory (EEPROM) is programmed in the system by using a 12 V or 5.0 V **programming pulse**.

SUMMARY

(*cont.*)

- Static RAM (SRAM) retains data for as long as the system power supply is attached.
- These memory types are available in sizes up to **128K x 8**.

SUMMARY

(*cont.*)

- Dynamic RAM (DRAM) retains data for only a short period, usually 2-4 ms.
- This creates problems for the memory system designer because the **DRAM must be refreshed periodically**.
- DRAMs also have multiplexed address inputs that require an external **multiplexer** to provide each half of the address at the appropriate time.

SUMMARY

(*cont.*)

- Memory address decoders select an EPROM or RAM at a particular area of the memory.
- Commonly found address decoders include the 74LS138 **3-to-8 line decoder**, the 74LS139 **2-to-4 line decoder**, and programmed selection logic in a PLD.

SUMMARY

(*cont.*)

- The access speed of the EPROM must be compatible with the microprocessor to which it is interfaced.
- Many EPROMs available today have an access time of 450 ns, which is too slow for the 5 MHz 8088.
- In order to circumvent this problem, a wait state is inserted to increase memory access time to 660 ns.

SUMMARY

(*cont.*)

- Error-correction features are also available for memory systems, but these require the storage of many more bits.
- If an 8-bit number is stored with an error-correction circuit, it actually takes 13 bits of memory: five for an error checking code and eight for the data.
- Most error-correction integrated circuits are able to correct only a single-bit error.

SUMMARY

- Dynamic RAM controllers are designed to control DRAM memory components.
- Many DRAM controllers today are **built into** the chip set and contain address multiplexers, refresh counters, and the circuitry required to do a periodic DRAM memory refresh.