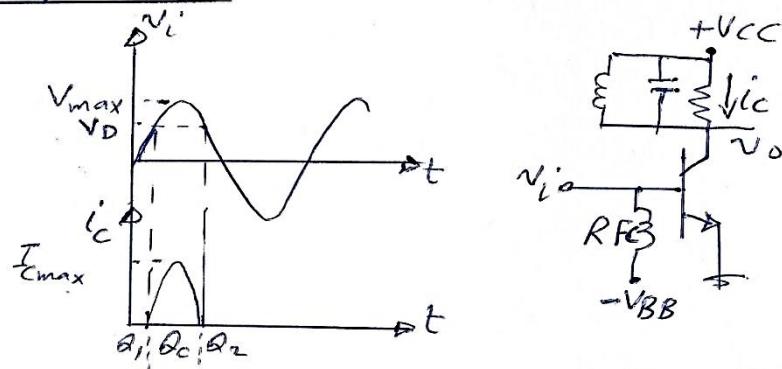


## Class-C Amplifier:

(12)



The amplifier conducts for angles less than  $180^\circ$ . This mode can have a great efficiency than Class B but it creates more distortion than class A or B amplifiers. This class is used in high frequency applications and high power. The RFC (Radio-Frequency Choke) has a high impedance at high frequency input and thereby prevents the dc source from shorting the ac input. The input must reach the level sufficient to overcome both the negative bias and \$V\_{BE}\$ drop.

$$V_D = |V_{BB}| + 0.7V$$

drop

A resonance network (LC tuning circuit) is used at the output to obtain only the fundamental frequency at the output and remove the other harmonics which have much smaller gain than the fundamental.

$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$i_c = \begin{cases} I_{c\max} \sin \omega t - I_D & \theta_1 \leq \omega t \leq \theta_2 \\ 0 & \text{otherwise} \end{cases}$$

(13)

$$I_D = I_{c\max} \sin \theta_1$$

Direct current is:

$$\begin{aligned} I_{(dc)} &= \frac{1}{T} \int_{\theta_1/\omega}^{\theta_2/\omega} (I_{c\max} \sin \omega t - I_D) dt \\ &= \frac{2 I_{c\max} \cos \theta_1 - I_D (\theta_2 - \theta_1)}{2\pi} \end{aligned}$$

$$\theta_C = 2\theta = \theta_2 - \theta_1$$

$$I_D = I_{c\max} \sin \theta_1 = I_{c\max} \sin(\frac{\pi}{2} - \theta) = I_{c\max} \cos \theta$$

$$I_{Cdc} = \frac{I_{c\max}}{\pi} (\sin \theta - \theta \cos \theta)$$

$$P_{CC} = V_{CC} I_{Cdc}$$

If the output turned to the fundamental frequency current pulse, then output power.

$$P_L = \frac{I_{1\max}^2 R_L}{2} = \left( \frac{I_{1\max}}{\sqrt{2}} \right)^2 R_L$$

Where  $I_{1\max}$  is the amplitude of the fundamental current component  $I_1 = \frac{4}{T} \int_0^{\theta_2/\omega} (I_{c\max} \cos \omega t - I_D) \cos \omega t dt$

$$I_1 = \frac{I_{c\max}}{2\pi} [2\theta - \sin 2\theta]$$

$$\eta = \frac{P_L}{P_{CC}} = \frac{I_{1\max}^2 R_L / 2}{V_{CC} I_{Cdc}}$$

$$|\eta_{\max}| = \frac{V_{CC} I_1}{2V_{CC} I_{Cdc}} = \frac{2\theta - \sin 2\theta}{4(\sin \theta - \theta \cos \theta)}$$

$$I_{1\max} = \frac{V_{CC}}{R_L}$$

$$P_C = P_{CC} - P_L$$

$$P_C = \frac{V_{CC} S_{Cmax}}{\pi} (\sin\theta - \alpha \cos\theta) - \frac{V_{CC}^2}{2R_L}$$

for max. output power 14

$$\frac{P_C}{P_L} = R_L \left( \frac{4(\sin\theta - \alpha \cos\theta)}{2\theta - \sin 2\theta} - 1 \right)$$

