

Q: For the circuit shown draw the ac equivalent circuit and find A_{vs} , A_i , Z_i and Z_o , where $h_{ie}=1\text{k}\Omega$, $h_{fe}=100$ then $h_{ib}=10\Omega$ for each transistor.

