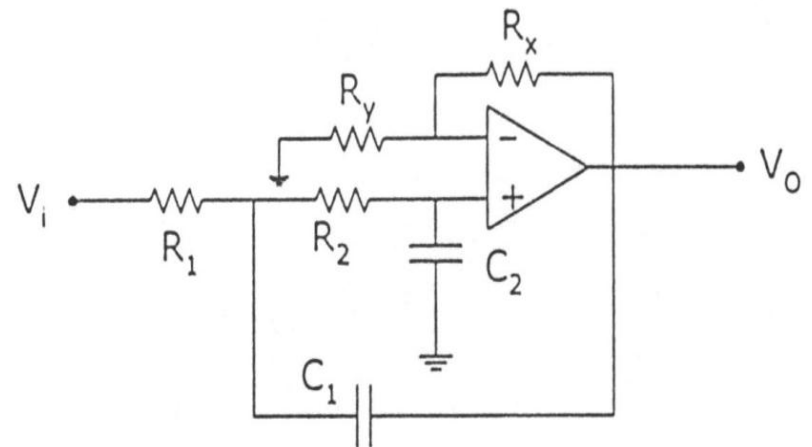


Active Filters

* *Active filter* is an electronic circuit consisting of an amplifier and other devices such as resistors and capacitors. In contrast, a *passive filter* is a circuit which consists of passive devices such as resistors, capacitors and inductors. Operational amplifiers are used extensively as active filters.

* A *low-pass filter* transmits (passes) all frequencies below a *critical (cutoff)* frequency denoted as ω_c ,

and *attenuates* (blocks) all frequencies above this cutoff frequency. An op amp low-pass filter is shown in the fig.:



* The frequency response *for amplitude* of a LPF. is shown in the figure below:


The straight vertical and horizontal lines represent the ideal (unrealizable) and the smooth curve represents the practical (realizable) low-pass filter characteristics. The vertical scale represents the magnitude of the ratio

of output-to-input voltage, $\frac{V_O}{V_I}$, that is

the gain G_v . The cutoff frequency ω_c is the frequency at which the maximum value of $\frac{V_O}{V_I}$ which is $G_{v_{max}}$,

(when $G_{v_{max}} = 1$, then the response is shown

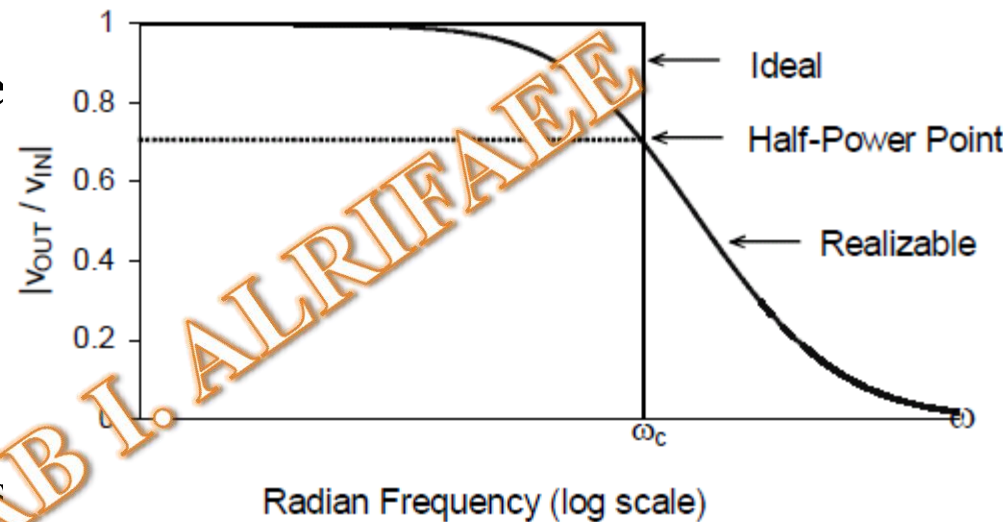as in the fig. above) falls to $0.707 G_{v_{max}}$, and this is the *half power* or the -3db point.



Filter design

- A general expression for the transfer function a 1st-order low pass filter can be written as: $A_v(s) = \frac{A_v(0)}{1 + \frac{s}{\omega_0}}$

The response to a steady state sinusoid is: $A_v(j\omega) = \frac{A_v(0)}{1 + \frac{j\omega}{\omega_0}}$

$$|A_v(j\omega)| = \frac{A_v(0)}{\left[1 + \left(\frac{\omega}{\omega_0}\right)^2\right]^{1/2}}$$
$$\phi = -\tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

low pass filter

2nd-order low pass filter transfer function is given by

$$A_v(s) = \frac{A_v(0)}{\frac{s^2}{\omega_0^2} + \frac{s}{Q\omega_0} + 1} \quad \dots\dots (1)$$

$$|A_V(j\omega)| = \frac{A_{v_0}}{\left[1 - \left(\frac{\omega^2}{\omega_0^2}\right)^2 + \frac{\omega^2}{\omega_0^2 Q^2}\right]^{1/2}} \dots\dots(2)$$

* The poles are the roots of the denominator polynomial given by

$$S_{1,2} = -\frac{\omega_0}{2Q} \pm \omega_0 \left[\left(\frac{1}{2Q}\right)^2 - 1 \right]^{1/2}$$

To design a 2nd-order LPF shown in the figure above, The transfer function of this circuit is given by:

$$A_V(S) = \frac{V_o}{V_i} = \frac{A_{v_0}}{S^2 R_1 R_2 C_1 C_2 + S[R_2 C_2 + R_1 C_2 + R_1 C_1(1 - A_{v_0})] + 1} \dots\dots\dots (3)$$

From comparing equation (1) and (3) and equating the coefficient of denominators, it's seen that

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \dots\dots\dots(4)$$

$$\frac{1}{Q} = \frac{R_2 C_2 + R_1 C_2 + R_1 C_1 (1 - A_{v_o})}{\sqrt{R_1 R_2 C_1 C_2}} \dots\dots\dots (5)$$

* Now, if $R_1 = R_2$, $C_1 = C_2$ then from equation (5):



$$\frac{1}{Q} = 3 - A_{V_o} \quad , \text{ for Butter worth response: } \frac{1}{Q} = \sqrt{2} \text{ , So}$$

$$1.414 = 3 - A_{V_o} \text{ and } A_{V_o} = 1.6$$

* The OP-AMP's gain can be set to give this ratio. However, if the gain of the amplifier is set at unity and $R_1 = R_2$ and $\frac{1}{Q} = \sqrt{2}$, from equation (5): $C_1 = ? C_2$.

* High Pass Filter

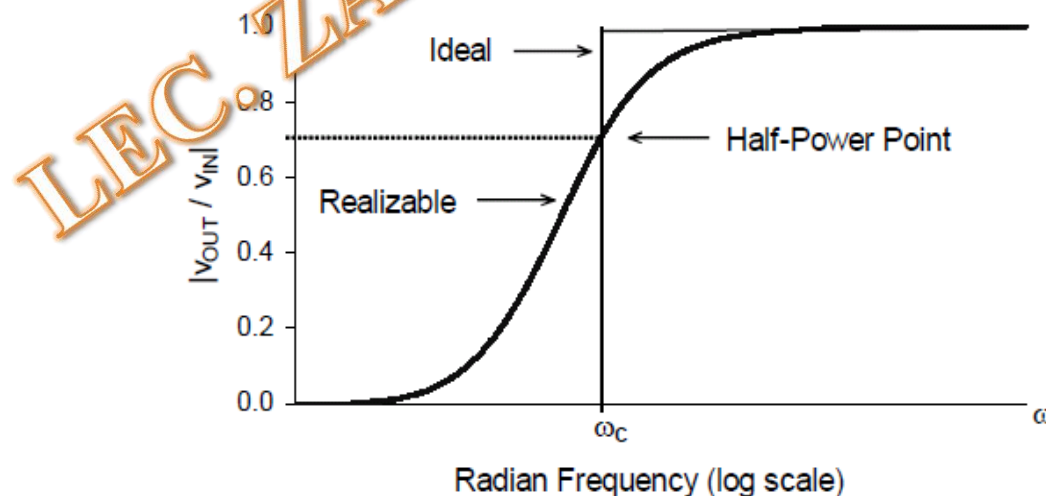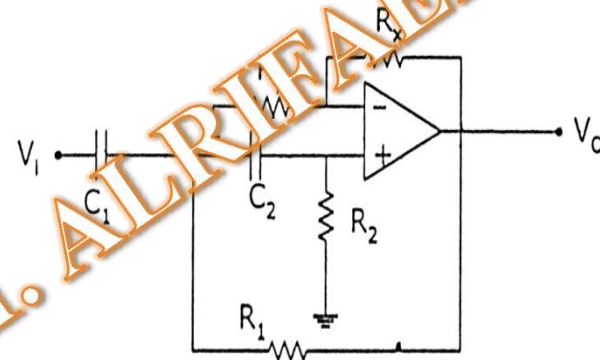- A *high-pass filter* transmits (passes) all frequencies above a critical (cutoff) frequency ω_c , and attenuates (blocks) all frequencies below the cutoff frequency. An op amp high-pass filter is shown in the Fig. and its frequency response in the fig.



HPF. Design

- A high pass 2nd-order filter can be obtained from the low pass 2nd-order of equation (1) by applying the transformation

$$\frac{S}{\omega_o} \Big|_{LP} \rightarrow \frac{\omega_o}{S} \Big|_{HP}$$


And the same design procedure is followed as before.

* Band Pass Filter

The general transfer function of a band pass filter is given by

$$A_v(S) = \frac{A_{V_o} \frac{\omega_o}{Q} S}{S^2 + \frac{\omega_o}{Q} S + \omega_o^2} \dots \dots \dots (1)$$
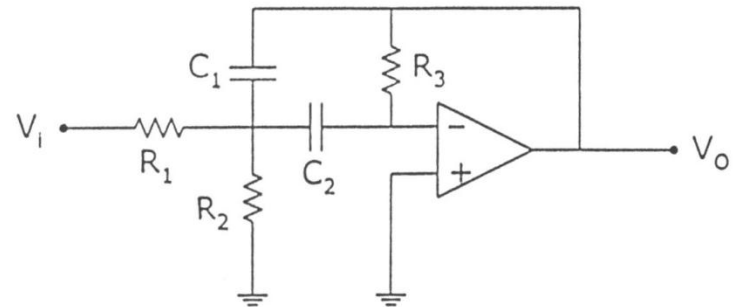
$$Q = \frac{\text{center frequency}}{\text{bandwidth}} = \frac{\omega_o}{\omega_1 - \omega_2}$$



where ω_1 and ω_2 are the upper and lower 3-dB points.

$$|A_{V(j\omega)}| = \frac{A_{V_o}}{\left[1+Q^2\left(\frac{\omega}{\omega_o}-\frac{\omega_o}{\omega}\right)^2\right]^{1/2}}, \text{ And } \phi = -\tan^{-1}\left[Q\left(\frac{\omega}{\omega_o}-\frac{\omega_o}{\omega}\right)\right]$$

If the band pass filter as on the fig. above is taken, the transfer function is given by

$$A_v(S) = \frac{\frac{S}{R_1 C_1}}{S^2 + \frac{C_1 + C_2}{R_3 C_1 C_2} S + \frac{1}{R R_3 C_1 C_2}} \dots (2)$$

Where $R' = R_1 / R_2$

- Equating the coefficients of equations (1) and (2) yields

$$R_1 C_1 = \frac{Q}{\omega_o A_{V_o}} \dots\dots\dots(3)$$

$$R_3 \frac{C_1 C_2}{C_1 + C_2} = \frac{Q}{\omega_o} \dots\dots\dots(4)$$

$$R' R_3 C_1 C_2 = \frac{1}{\omega_o^2} \dots\dots\dots(5)$$

From equations (8) to (10) the values of R_1 , R_3 , R' , C_1 and C_2 can be obtained from specific value of ω_o , Q , and A_{V_o} .

Since we have only three equations for the five parameters, two of these (say C_1 and C_2) may be chosen arbitrary.

*Band Reject Filter

- A band reject filter can be constructed by connecting the low and high pass filter sections in parallel and summing their outputs, as shown in the figure below.

